


To check whether there are input disks or not

To identify the disc when sorting


Additional sensor for any need, maybe for use in the gripper

Buzzer / Speaker

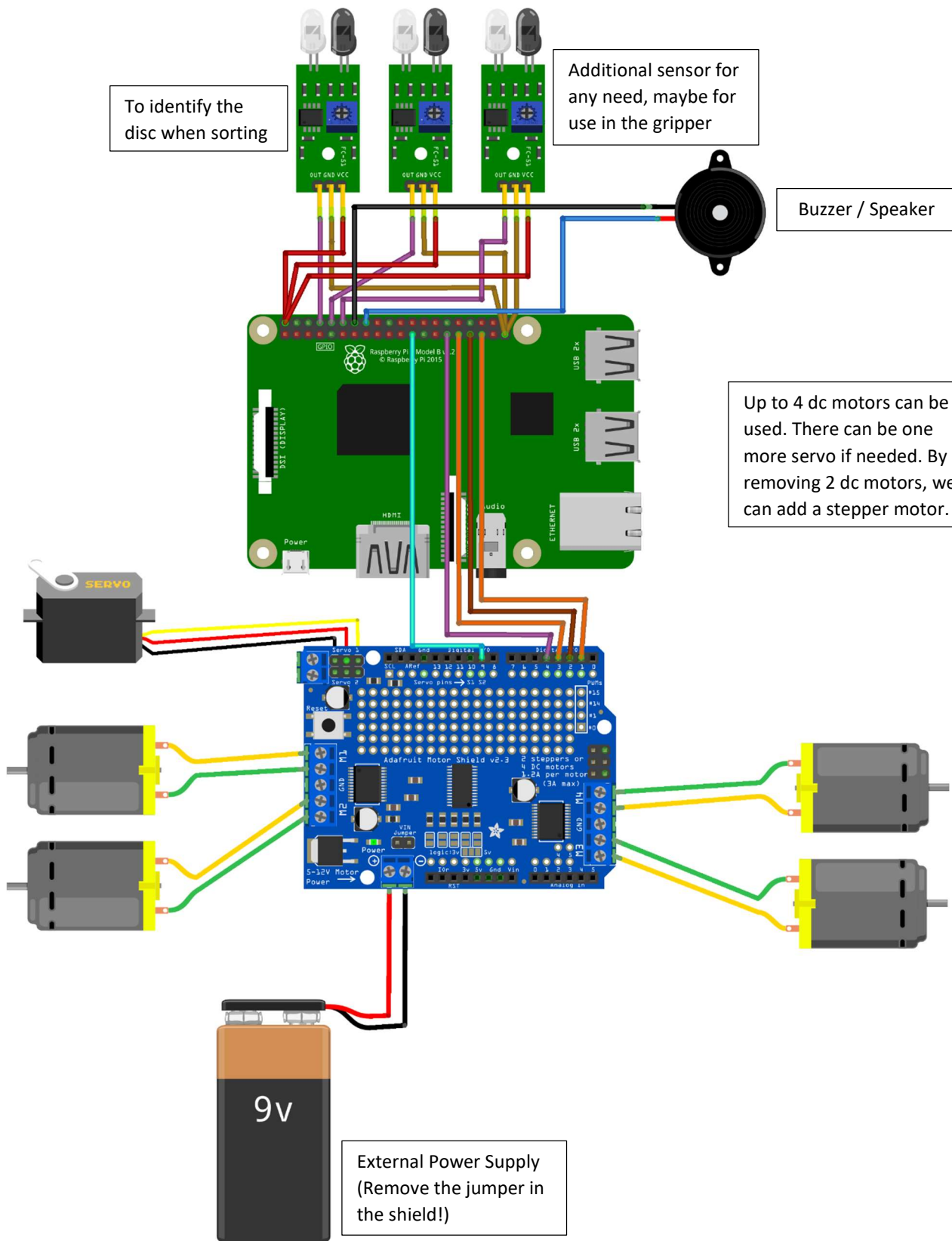Up to 4 dc motors can be used. There can be one more servo if needed. By removing 2 dc motors, we can add a stepper motor.



Circuit Schema

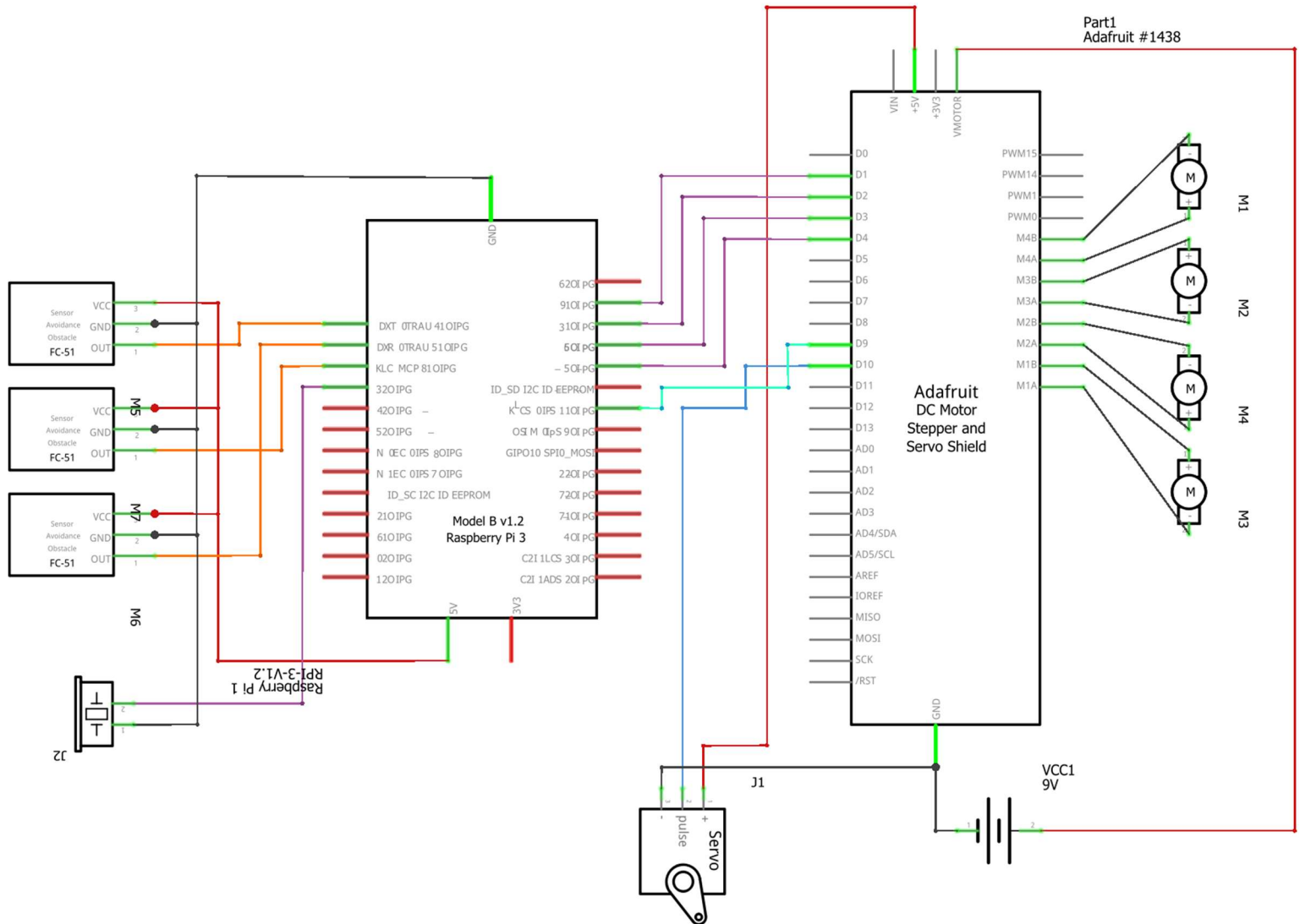

fritzing